



Sr. No.	Parameter	HWR	FWR	Bridge rectifier
12.	Transformer core saturation	Possible	Not possible	Not possible
13.	PIV	V_m	$2 V_m$	V_m
14.	Expression for the peak load current	$I_m = \frac{V_m}{(R_S + R_F + R_L)}$	$I_m = \frac{V_m}{(R_S + R_F + R_L)}$	$I_m = \frac{V_m}{(R_S + 2 R_F + R_L)}$
15.	Circuit diagram	Refer Fig. A	Refer Fig. B	Refer Fig. C

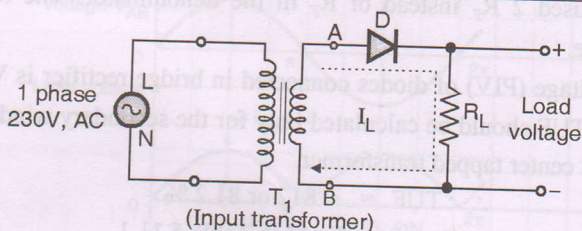


Fig. A : HWR

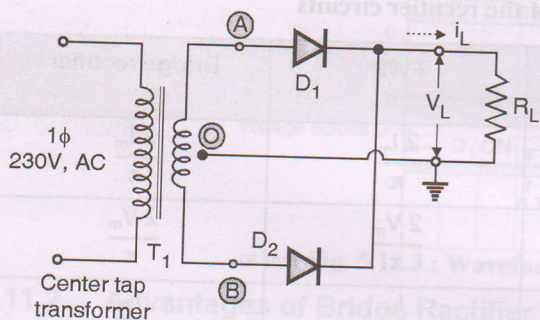


Fig. B : FWR

(F-2266)

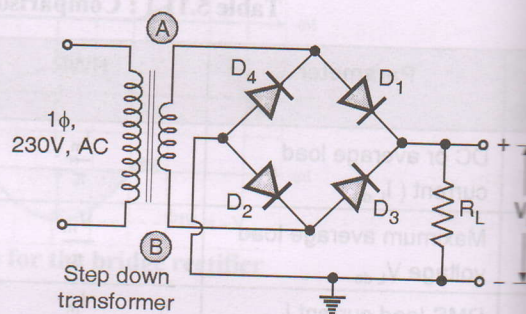


Fig. C : Bridge

5.11.6 Examples on Bridge Rectifier :

Ex. 5.11.1 : A bridge rectifier circuit has secondary voltage of $12 V_{rms}$. Assume secondary resistance and diode forward resistance to be negligible. Load resistance is 100Ω . Calculate peak load current, DC load current, rms load current and PIV across each diode.

Soln. : Given : $V_{S rms} = 12 V$, $R_S = 0 \Omega$, $R_F = 0 \Omega$, $R_L = 100 \Omega$.

1. Peak load current, $I_m = \frac{V_m}{(R_S + 2 R_F + R_L)} = \frac{\sqrt{2} V_{S rms}}{R_L}$

$\therefore I_m = \frac{\sqrt{2} \times 12}{100} = 0.169 \text{ Amp}$

...Ans.

2. D.C. load current, $I_{L dc} = \frac{2 I_m}{\pi} = \frac{2 \times 0.169}{\pi} = 0.108 \text{ Amp}$

...Ans.



$$3. \quad \text{RMS load current, } I_{L \text{ rms}} = \frac{I_m}{\sqrt{2}} = \frac{0.169}{\sqrt{2}} = 0.118 \text{ Amp}$$

...Ans.

$$4. \quad \text{PIV across each diode, PIV} = V_m = \sqrt{2} \times 12 = 16.97 \text{ V}$$

...Ans.

Ex. 5.11.2 : A bridge rectifier is applied with input from a step down transformer having turns ratio 8:1 and input 230 V, 50 Hz. If the diode forward resistance is 1Ω , secondary resistance is 10Ω and load resistance connected is $2 \text{ k}\Omega$ find :



1. DC power output
2. PIV across each diode
3. % efficiency
4. % regulation at full load

Refer CD for Solution

Ex. 5.11.3 : Determine the rms value of secondary voltage of a transformer which provides 9 V dc output voltage when connected to a bridge rectifier. If the secondary winding resistance is 3Ω and diode forward resistance is 1Ω what will be the output voltage when 90Ω load is connected to the power supply ?



Refer CD for Solution

Ex. 5.11.4 : A full wave bridge rectifier is supplied from 230 V, 50 Hz and uses a transformer of turns ratio of 15 : 1. It uses load resistance of 50Ω . Calculate load voltage and ripple voltage. Assume ideal diode and transformer. Assume standard value of ripple factor for full wave rectifier.



Refer CD for Solution

Ex. 5.11.5 : A $5 \text{ k}\Omega$ load is fed from a bridge rectifier connected with a transformer secondary whose primary is connected to 460V, 50 Hz supply. The ratio of number of primary to secondary turns is 2 : 1. Calculate dc load current, dc load voltage, ripple voltage and PIV rating of diode.

Dec. 10, 4 Marks.

Soln. :

Given : $N_p : N_s = 2 : 1$, $R_L = 5 \text{ k}\Omega$, Assume R_s and $R_F = 0$

$$1. \quad \text{Rms secondary voltage } V_{\text{srms}} = \frac{N_s}{N_p} \times 460 = \frac{1}{2} \times 460 = 230 \text{ V.} \quad \dots(1)$$

$$2. \quad \text{Peak secondary voltage } V_m = \sqrt{2} \times V_{\text{srms}} = \sqrt{2} \times 230 = 325.26 \quad \dots(2)$$

$$3. \quad \text{Peak load current } I_m = \frac{V_m}{R_s + 2R_F + R_L} = \frac{325.26}{5000} = 0.065 \text{ A.} \quad \dots(3)$$

$$4. \quad \text{DC load current } I_{Ldc} = \frac{2I_m}{\pi} = \frac{2 \times 0.065}{\pi} = 0.041 \quad \dots\text{Ans.}$$

$$5. \quad \text{DC load voltage } V_{Ldc} = I_{Ldc} \times R_L = 0.041 \times 5000 = 205 \text{ V.} \quad \dots\text{Ans.}$$

$$6. \quad \text{Ripple voltage} = \text{Ripple factor} \times V_{Ldc}$$

The standard value of ripple factor is 0.482 for the bridge rectifier.

$$\therefore \text{Ripple voltage} = 0.482 \times 205 = 98.81 \text{ V} \quad \dots\text{Ans.}$$

$$7. \quad \text{PIV rating of diode PIV} = V_m = 325.26 \text{ V} \quad \dots\text{Ans.}$$